

Computer Architecture

Lab 4 Report

Name:	Asudy Wang 王浚哲	Student ID:	3180103011	Major:	Computer Science & Technology
Course:	Computer Architecture		Place:	Room 301, Cao Guangbiao Building West Wing, Yuquan Campus	
Due Date:	2020-12-28	Groupmate:	Flaze He	Instructor:	Kai Bu

Table of Contents

Table of Contents

Lab 4. Pipelined CPU with Forwarding

- §1 Purposes & Requirements
 - 1.1 Experiment Purpose
 - 1.2 Experiment Tasks
- §2 Contents & Principles
 - 2.1 Data Hazard Stalls
 - 2.2 Datapath
 - 2.3 Controller
- §3 Main Instruments & Materials
 - 3.1 Experiment Instruments
 - 3.2 Experiment Materials
- §4 Experiment Procedure & Operations
 - 4.1 Modify *datapath.v*
 - 4.2 Modify *controller.v*
 - 4.3 Verify the Forwarding Design
- §5 Results & Analysis
 - 5.1 Function Verification
- §6 Discussion & Experience
- Appendix A. *controller.v*
- Appendix B. *datapath.v*

Lab 4. Pipelined CPU with Forwarding

§1 Purposes & Requirements

1.1 Experiment Purpose

- Understand the principles of **Pipelined CPU Bypass Unit**.
- Master the method of Pipelined Pipeline **Forwarding Detection** and Pipeline **Forwards**.
- Master the Condition In which Pipeline Forwards.
- Master the Condition In which Bypass Unit doesn't Work and the Pipeline **stalls**.
- Master methods of program verification of Pipelined CPU with forwarding.


1.2 Experiment Tasks

- Design the **Bypass Unit** in datapath of the 5-staged Pipelined CPU.
- **Modify the CPU Controller**
 - Conditions in which the pipeline *forwards*.
 - Conditions in which the pipeline *Stalls*.
- **Verify** the Pipelined CPU with program and observe the execution of the program.

§2 Contents & Principles

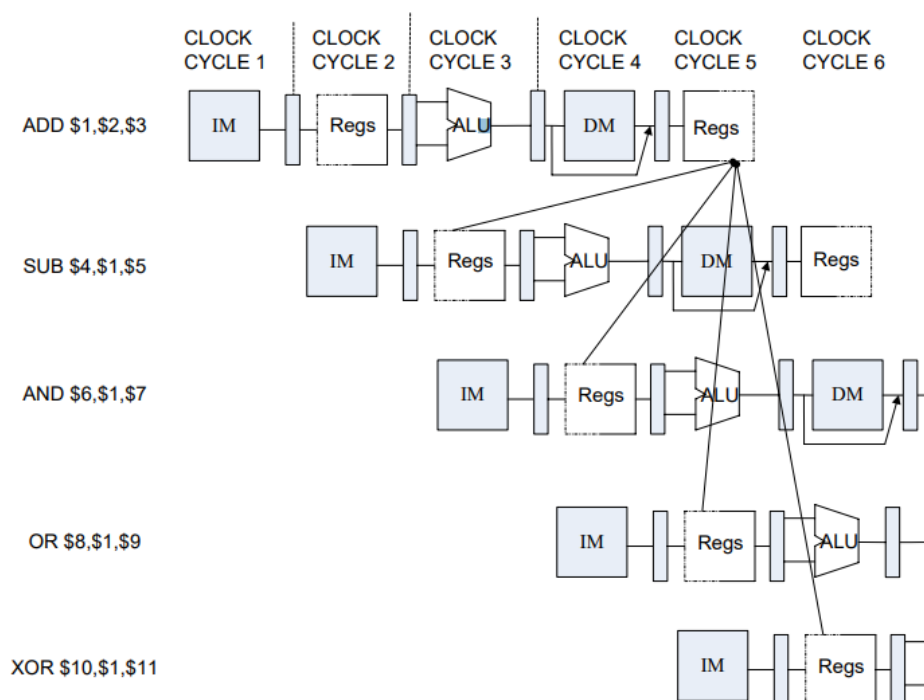
2.1 Data Hazard Stalls

- Data hazards happen mostly because that one instruction is reading a register which is NOT written back by the previous instruction yet. For example, in the following figure, the value of register **\$1** is required by all instructions except the first one.




In this case, our pipeline will have to **stall** until the result of the first instruction is written back to register **\$1** (if we don't have a design for forwarding).

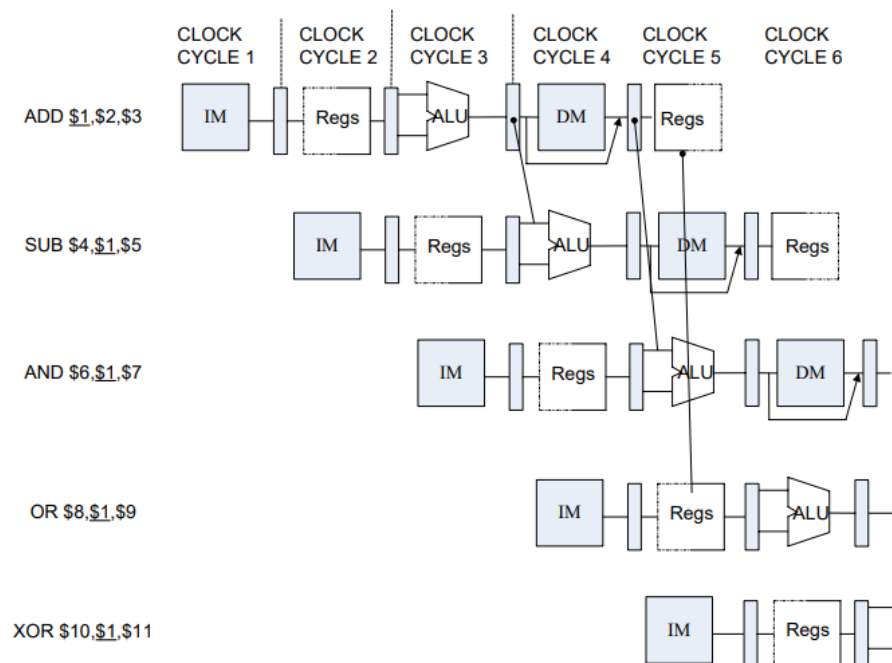- We can minimize *Data Hazard Stalls* by using **Forwarding**: transfer the needed (correct) data to other stages in the datapath even if the current instruction isn't finished. In most cases, the data hazard can be resolved by Forwarding (also called *bypassing*, or *short-circuiting*).




We can find that this time the pipeline isn't stalling.

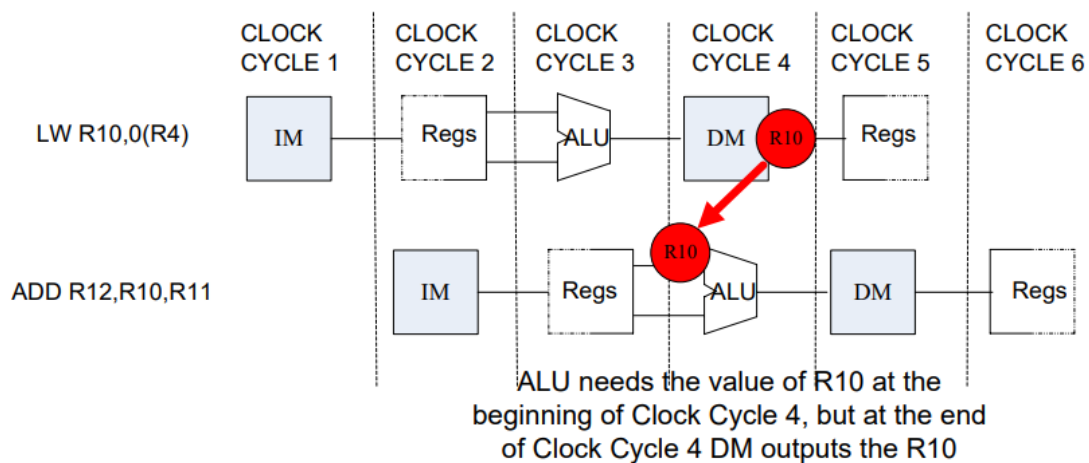- However, in some cases, data hazards can NOT be resolved by Forwarding and require pipeline stalls.



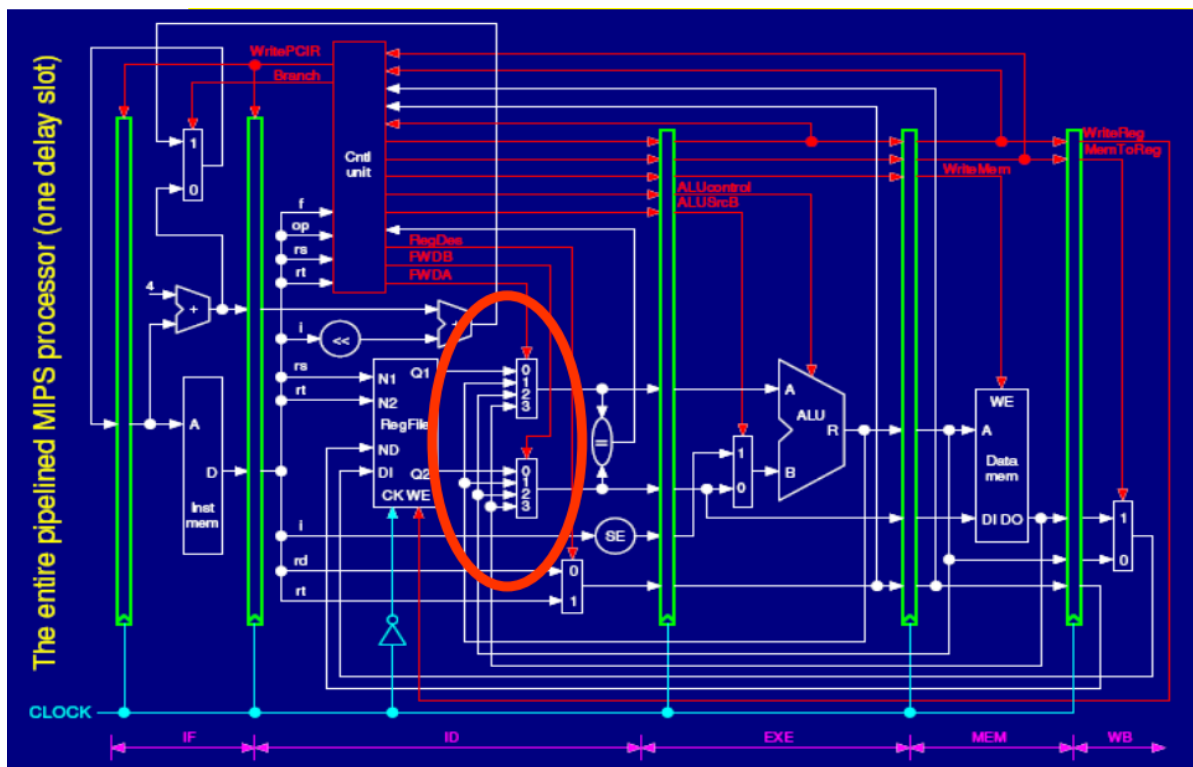2.2 Datapath

The schematic of the modified datapath is shown in the following figure:



There're 3 parts to be added in order to implement pipeline forwarding:

1. *rs* data read from the register file (forwarded to ID stage).
2. *rt* data read from the register file (forwarded to ID stage).
3. Memory in/out forwarding.

2.3 Controller

To implement forwarding and make the additional components of the new datapath work as expected, some control signals need to be added to select the sources.

The relationship between control signals and MUXs is shown in the above figure as well.

§3 Main Instruments & Materials

3.1 Experiment Instruments

1. A Computer with ISE 14.7 Installed
2. SWORD Board

3.2 Experiment Materials

None.

§4 Experiment Procedure & Operations

4.1 Modify *datapath.v*

Add the 3 forwarding wires & MUXs to the datapath.

1. In **ID stage**, add *rs* and *rt* source selection:

```
1  reg [31:0] data_rs_fwd, data_rt_fwd;
2
3  always @(*) begin
4      data_rs_fwd = data_rs;
5      data_rt_fwd = data_rt;
6      case (fwd_a_ctrl)
7          0: data_rs_fwd = data_rs;
8          1: data_rs_fwd = alu_out_exe;
9          2: data_rs_fwd = alu_out_mem;
10         3: data_rs_fwd = mem_din;
11     endcase
12     case (fwd_b_ctrl)
13         0: data_rt_fwd = data_rt;
14         1: data_rt_fwd = alu_out_exe;
15         2: data_rt_fwd = alu_out_mem;
16         3: data_rt_fwd = mem_din;
17     endcase
18     rs_rt_equal = (data_rs_fwd == data_rt_fwd);
19 end
```

2. In **MEM stage**, add memory source selection:

```
1  // MEM stage
2  always @(posedge clk) begin
3      if (mem_rst) begin
4          mem_valid <= 0;
5          inst_addr_mem <= 0;
6          inst_data_mem <= 0;
7          regw_addr_mem <= 0;
8          data_rt_mem <= 0;
9          alu_out_mem <= 0;
10         mem_ren_mem <= 0;
11         mem_wen_mem <= 0;
12         wb_data_src_mem <= 0;
13         wb_wen_mem <= 0;
14         fwd_m_mem <= 0;
15         is_load_mem <= 0;
16     end
17     else if (mem_en) begin
18         mem_valid <= exe_valid;
19         inst_addr_mem <= inst_addr_exe;
20         inst_data_mem <= inst_data_exe;
21         regw_addr_mem <= regw_addr_exe;
22         data_rt_mem <= data_rt_exe;
23         alu_out_mem <= alu_out_exe;
24         mem_ren_mem <= mem_ren_exe;
25         mem_wen_mem <= mem_wen_exe;
26         wb_data_src_mem <= wb_data_src_exe;
27         wb_wen_mem <= wb_wen_exe;
28         fwd_m_mem <= fwd_m_exe;
29         is_load_mem <= is_load_exe;
```

```

30     end
31 end
32
33 assign
34     mem_ren = mem_ren_mem,
35     mem_wen = mem_wen_mem,
36     mem_addr = alu_out_mem,
37     mem_dout = fwd_m_mem ? regw_data_wb : data_rt_mem; // Memory source
selection

```

4.2 Modify *controller.v*

Add **Forwarding Control** to the pipeline control of the controller.

```

1  always @(*) begin
2      reg_stall = 0;
3      fwd_a = 0;
4      fwd_b = 0;
5      fwd_m = 0;
6      if (rs_used && addr_rs != 0) begin
7          if (regw_addr_exe == addr_rs && wb_wen_exe) begin
8              if (is_load_exe)
9                  reg_stall = 1;
10             else
11                 fwd_a = 1;
12             end
13             else if (regw_addr_mem == addr_rs && wb_wen_mem) begin
14                 if (is_load_mem)
15                     fwd_a = 3;
16                 else
17                     fwd_a = 2;
18             end
19         end
20         if (rt_used && addr_rt != 0) begin
21             if (regw_addr_exe == addr_rt && wb_wen_exe) begin
22                 if (is_load_exe) begin
23                     if (is_store)
24                         fwd_m = 1;
25                     else
26                         reg_stall = 1;
27                 end
28                 else
29                     fwd_b = 1;
30             end
31             else if (regw_addr_mem == addr_rt && wb_wen_mem) begin
32                 if (is_load_mem)
33                     fwd_b = 3;
34                 else
35                     fwd_b = 2;
36             end
37         end
38     end
end

```

4.3 Verify the Forwarding Design

1. Use the program provided by the template (`inst_mem.hex`) to verify the implementation of our *Pipelined CPU*. The code is provided in hexadecimal, which is very difficult for humans to understand. Converting it to something human-readable using a disassembler is a great idea. The translated program (in MIPS) is as the following:


```
code > ASM inst_mem.asm
1  and $at $zero $zero
2  ori $a0 $at 80
3  addi $a1 $zero 4
4  jal 10
5  sw $v0 0($a0)
6  lw $t1 0($a0)
7  sw $t1 4($a0)
8  sub $t0 $t1 $a0
9  j 8
10 sll $zero $zero 0
11 add $t0 $zero $zero
12 lw $t1 0($a0)
13 add $t0 $t0 $t1
14 addi $a1 $a1 -1
15 addi $a0 $a0 4
16 slt $v1 $zero $a1
17 bne $v1 $zero -6
18 or $v0 $t0 $zero
19 jr $ra
```

2. Open the *ISE Project* and *Generate Programming File* of the top module, then upload the *.bit* file to the SWORD board to see whether our pipelined CPU works as desired.

§5 Results & Analysis

5.1 Function Verification

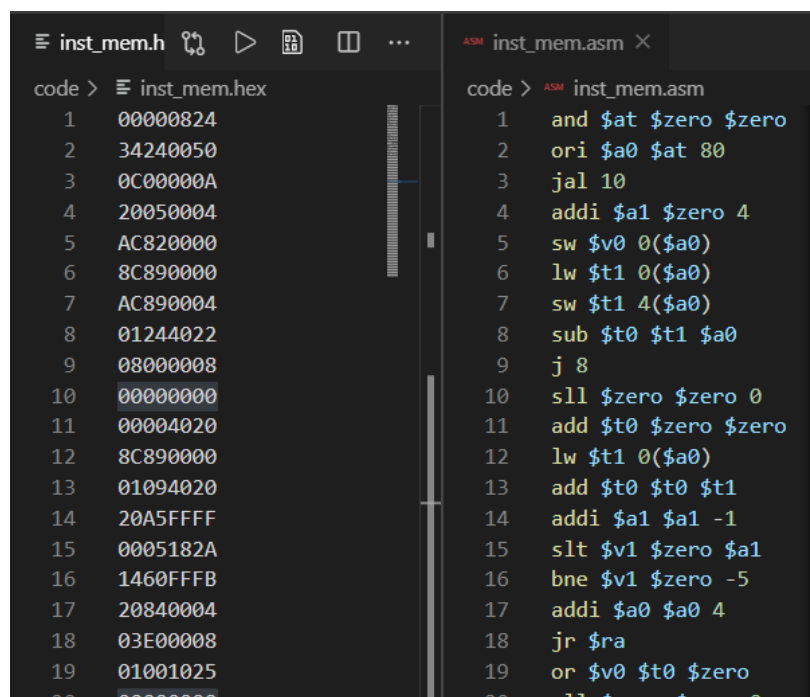1. The hexadecimal file used to verify the design and its MIPS assembly comparison is show in the following figure:



2. The *Programming File* of the top module was **successfully generated and uploaded** to the SWORD board.
3. Turning on `SW[0]` on board makes the CPU enter *single-step debug* mode, during which time the *bottom-left* `BTN` makes it step forward. All debug information is shown on the *VGA display* connected to the board.

You can refer to the *appended video clip* for the full execution progress of the above program.

- When executing instruction 2 (`ori $a0 $at 80`) **without the forwarding components**, the pipeline would *stall* since it reads `$at`, which is the destination register of the previous instruction.
 - **After we added the forwarding support** to the pipeline, however, the pipeline *didn't stall* while executing instruction `ori $a0 $at 80`. That means that our forwarding design worked.
4. According to our observation, the program was executed **as desired** on the SWORD board. **We concluded that our *Pipelined CPU* was working as expected.**

§6 Discussion & Experience

In this lab course, I understood the principles of *pipeline forwarding* and took it into practice. I successfully implemented the Pipeline Forwarding Detection & Control components under the help of online tutorials and the help of my friends.

Appendix A. *controller.v*

```
1  `include "define.vh"
2
3  module controller (/*AUTOARG*/
4      input wire clk, // main clock
5      input wire rst, // synchronous reset
6      // debug
7      `ifdef DEBUG
8          input wire debug_en, // debug enable
9          input wire debug_step, // debug step clock
10         `endif
11         // instruction decode
12         input wire [31:0] inst, // instruction
13         input wire rs_rt_equal, // whether data from RS and RT are equal
14         input wire is_load_exe, // whether instruction in EXE stage is load
15         instruction
16         input wire [4:0] regw_addr_exe, // register write address from EXE
17         stage
18         input wire wb_wen_exe, // register write enable signal feedback from
19         EXE stage
20         input wire is_load_mem, // whether instruction in MEM stage is load
21         instruction
22         input wire [4:0] regw_addr_mem, // register write address from MEM
23         stage
24         input wire wb_wen_mem, // register write enable signal feedback from
25         MEM stage
26         output reg [1:0] pc_src, // how would PC change to next
27         output reg imm_ext, // whether using sign extended to immediate data
28         output reg [1:0] exe_a_src, // data source of operand A for ALU
29         output reg [1:0] exe_b_src, // data source of operand B for ALU
30         output reg [3:0] exe_alu_oper, // ALU operation type
31         output reg mem_ren, // memory read enable signal
32         output reg mem_wen, // memory write enable signal
33         output reg [1:0] wb_addr_src, // address source to write data back to
34         registers
35         output reg wb_data_src, // data source of data being written back to
36         registers
37         output reg wb_wen, // register write enable signal
38         output reg [1:0] fwd_a, // forwarding selection for channel A
39         output reg [1:0] fwd_b, // forwarding selection for channel B
40         output reg fwd_m, // forwarding selection for memory
41         output reg is_load, // whether current instruction is load instruction
42         output reg unrecognized, // whether current instruction can not be
43         recognized
44         // pipeline control
45         output reg if_rst, // stage reset signal
46         output reg if_en, // stage enable signal
47         input wire if_valid, // stage valid flag
48         output reg id_rst,
49         output reg id_en,
50         input wire id_valid,
51         output reg exe_rst,
52         output reg exe_en,
53         input wire exe_valid,
54         output reg mem_rst,
```

```

46     output reg mem_en,
47     input wire mem_valid,
48     output reg wb_rst,
49     output reg wb_en,
50     input wire wb_valid
51 );
52
53 `include "mips_define.vh"
54
55 // instruction decode
56 reg rs_used, rt_used;
57 reg is_store;
58
59 always @(*) begin
60     pc_src = PC_NEXT;
61     imm_ext = 0;
62     exe_a_src = EXE_A_RS;
63     exe_b_src = EXE_B_RT;
64     exe_alu_oper = EXE_ALU_ADD;
65     mem_ren = 0;
66     mem_wen = 0;
67     wb_addr_src = WB_ADDR_RD;
68     wb_data_src = WB_DATA_ALU;
69     wb_wen = 0;
70     rs_used = 0;
71     rt_used = 0;
72     is_load = 0;
73     is_store = 0;
74     unrecognized = 0;
75     case (inst[31:26])
76         INST_R: begin
77             case (inst[5:0])
78                 R_FUNC_JR: begin
79                     pc_src = PC_JR;
80                     rs_used = 1;
81                 end
82                 R_FUNC_ADD: begin
83                     exe_alu_oper = EXE_ALU_ADD;
84                     wb_addr_src = WB_ADDR_RD;
85                     wb_data_src = WB_DATA_ALU;
86                     wb_wen = 1;
87                     rs_used = 1;
88                     rt_used = 1;
89                 end
90                 R_FUNC_SUB: begin
91                     exe_alu_oper = EXE_ALU_SUB;
92                     wb_addr_src = WB_ADDR_RD;
93                     wb_data_src = WB_DATA_ALU;
94                     wb_wen = 1;
95                     rs_used = 1;
96                     rt_used = 1;
97                 end
98                 R_FUNC_AND: begin
99                     exe_alu_oper = EXE_ALU_AND;
100                    wb_addr_src = WB_ADDR_RD;
101                    wb_data_src = WB_DATA_ALU;
102                    wb_wen = 1;
103                    rs_used = 1;

```

```

104         rt_used = 1;
105     end
106     R_FUNC_OR: begin
107         exe_alu_oper = EXE_ALU_OR;
108         wb_addr_src = WB_ADDR_RD;
109         wb_data_src = WB_DATA_ALU;
110         wb_wen = 1;
111         rs_used = 1;
112         rt_used = 1;
113     end
114     R_FUNC_SLT: begin
115         exe_alu_oper = EXE_ALU_SLT;
116         wb_addr_src = WB_ADDR_RD;
117         wb_data_src = WB_DATA_ALU;
118         wb_wen = 1;
119         rs_used = 1;
120         rt_used = 1;
121     end
122     default: begin
123         unrecognized = 1;
124     end
125 endcase
126 end
127 INST_J: begin
128     pc_src = PC_JUMP;
129 end
130 INST_JAL: begin
131     pc_src = PC_JUMP;
132     exe_a_src = EXE_A_LINK;
133     exe_b_src = EXE_B_LINK;
134     exe_alu_oper = EXE_ALU_ADD;
135     wb_addr_src = WB_ADDR_LINK;
136     wb_data_src = WB_DATA_ALU;
137     wb_wen = 1;
138 end
139 INST_BEQ: begin
140     if (rs_rt_equal) begin
141         pc_src = PC_BRANCH;
142     end
143     imm_ext = 1;
144     rs_used = 1;
145     rt_used = 1;
146 end
147 INST_BNE: begin
148     if (~rs_rt_equal) begin
149         pc_src = PC_BRANCH;
150     end
151     imm_ext = 1;
152     rs_used = 1;
153     rt_used = 1;
154 end
155 INST_ADDI: begin
156     imm_ext = 1;
157     exe_b_src = EXE_B_IMM;
158     exe_alu_oper = EXE_ALU_ADD;
159     wb_addr_src = WB_ADDR_RT;
160     wb_data_src = WB_DATA_ALU;
161     wb_wen = 1;

```

```

162         rs_used = 1;
163     end
164     INST_ANDI: begin
165         imm_ext = 0;
166         exe_b_src = EXE_B_IMM;
167         exe_alu_oper = EXE_ALU_AND;
168         wb_addr_src = WB_ADDR_RT;
169         wb_data_src = WB_DATA_ALU;
170         wb_wen = 1;
171         rs_used = 1;
172     end
173     INST_ORI: begin
174         imm_ext = 0;
175         exe_b_src = EXE_B_IMM;
176         exe_alu_oper = EXE_ALU_OR;
177         wb_addr_src = WB_ADDR_RT;
178         wb_data_src = WB_DATA_ALU;
179         wb_wen = 1;
180         rs_used = 1;
181     end
182     INST_LW: begin
183         imm_ext = 1;
184         exe_b_src = EXE_B_IMM;
185         exe_alu_oper = EXE_ALU_ADD;
186         mem_ren = 1;
187         wb_addr_src = WB_ADDR_RT;
188         wb_data_src = WB_DATA_MEM;
189         wb_wen = 1;
190         is_load = 1;
191         rs_used = 1;
192     end
193     INST_SW: begin
194         imm_ext = 1;
195         exe_b_src = EXE_B_IMM;
196         exe_alu_oper = EXE_ALU_ADD;
197         mem_wen = 1;
198         is_store = 1;
199         rs_used = 1;
200         rt_used = 1;
201     end
202     default: begin
203         unrecognized = 1;
204     end
205 endcase
206 end
207
208 // pipeline control
209 reg reg_stall = 0;
210 wire [4:0] addr_rs, addr_rt;
211
212 assign
213     addr_rs = inst[25:21],
214     addr_rt = inst[20:16];
215
216 always @(*) begin
217     reg_stall = 0;
218     fwd_a = 0;
219     fwd_b = 0;

```

```

220     fwd_m = 0;
221     if (rs_used && addr_rs != 0) begin
222         if (regw_addr_exe == addr_rs && wb_wen_exe) begin
223             if (is_load_exe)
224                 reg_stall = 1;
225             else
226                 fwd_a = 1;
227         end
228         else if (regw_addr_mem == addr_rs && wb_wen_mem) begin
229             if (is_load_mem)
230                 fwd_a = 3;
231             else
232                 fwd_a = 2;
233         end
234     end
235     if (rt_used && addr_rt != 0) begin
236         if (regw_addr_exe == addr_rt && wb_wen_exe) begin
237             if (is_load_exe) begin
238                 if (is_store)
239                     fwd_m = 1;
240                 else
241                     reg_stall = 1;
242             end
243             else
244                 fwd_b = 1;
245         end
246         else if (regw_addr_mem == addr_rt && wb_wen_mem) begin
247             if (is_load_mem)
248                 fwd_b = 3;
249             else
250                 fwd_b = 2;
251         end
252     end
253 end
254
255 `ifdef DEBUG
256 reg debug_step_prev;
257
258 always @(posedge clk) begin
259     debug_step_prev <= debug_step;
260 end
261 `endif
262
263 always @(*) begin
264     if_rst = 0;
265     if_en = 1;
266     id_rst = 0;
267     id_en = 1;
268     exe_rst = 0;
269     exe_en = 1;
270     mem_rst = 0;
271     mem_en = 1;
272     wb_rst = 0;
273     wb_en = 1;
274     if (rst) begin
275         if_rst = 1;
276         id_rst = 1;
277         exe_rst = 1;

```

```

278         mem_rst = 1;
279         wb_rst = 1;
280     end
281     `ifdef DEBUG
282     // suspend and step execution
283     else if ((debug_en) && ~(~debug_step_prev && debug_step)) begin
284         if_en = 0;
285         id_en = 0;
286         exe_en = 0;
287         mem_en = 0;
288         wb_en = 0;
289     end
290     `endif
291     // this stall indicate that ID is waiting for previous LW
instruction, should insert one NOP between ID and EXE.
292     else if (reg_stall) begin
293         if_en = 0;
294         id_en = 0;
295         exe_rst = 1;
296     end
297 end
298
299 endmodule

```

Appendix B. *datapath.v*

```
1  `include "define.vh"
2
3  module datapath (
4      input wire clk, // main clock
5      // debug
6      `ifdef DEBUG
7          input wire [5:0] debug_addr, // debug address
8          output wire [31:0] debug_data, // debug data
9      `endif
10     // control signals
11     output reg [31:0] inst_data_id, // instruction
12     output reg rs_rt_equal, // whether data from RS and RT are equal
13     output reg is_load_exe, // whether instruction in EXE stage is load
14     instruction
15     output reg [4:0] regw_addr_exe, // register write address from EXE
16     stage
17     output reg wb_wen_exe, // register write enable signal feedback from
18     EXE stage
19     output reg is_load_mem, // whether instruction in MEM stage is load
20     instruction
21     output reg [4:0] regw_addr_mem, // register write address from MEM
22     stage
23     output reg wb_wen_mem, // register write enable signal feedback from
24     MEM stage
25     input wire [1:0] pc_src_ctrl, // how would PC change to next
26     input wire imm_ext_ctrl, // whether using sign extended to immediate
27     data
28     input wire [1:0] exe_a_src_ctrl, // data source of operand A for ALU
29     input wire [1:0] exe_b_src_ctrl, // data source of operand B for ALU
30     input wire [3:0] exe_alu_oper_ctrl, // ALU operation type
31     input wire mem_ren_ctrl, // memory read enable signal
32     input wire mem_wen_ctrl, // memory write enable signal
33     input wire [1:0] wb_addr_src_ctrl, // address source to write data
34     back to registers
35     input wire wb_data_src_ctrl, // data source of data being written back
36     to registers
37     input wire wb_wen_ctrl, // register write enable signal
38     input wire [1:0] fwd_a_ctrl, // forwarding selection for channel A
39     input wire [1:0] fwd_b_ctrl, // forwarding selection for channel B
40     input wire fwd_m_ctrl, // forwarding selection for memory
41     input wire is_load_ctrl, // whether current instruction is load
42     instruction
43     // IF signals
44     input wire if_rst, // stage reset signal
45     input wire if_en, // stage enable signal
46     output reg if_valid, // working flag
47     output reg inst_ren, // instruction read enable signal
48     output reg [31:0] inst_addr, // address of instruction needed
49     input wire [31:0] inst_data, // instruction fetched
50     // ID signals
51     input wire id_rst,
52     input wire id_en,
53     output reg id_valid,
54     // EXE signals
```

```

45     input wire exe_rst,
46     input wire exe_en,
47     output reg exe_valid,
48     // MEM signals
49     input wire mem_rst,
50     input wire mem_en,
51     output reg mem_valid,
52     output wire mem_ren, // memory read enable signal
53     output wire mem_wen, // memory write enable signal
54     output wire [31:0] mem_addr, // address of memory
55     output wire [31:0] mem_dout, // data writing to memory
56     input wire [31:0] mem_din, // data read from memory
57     // WB signals
58     input wire wb_rst,
59     input wire wb_en,
60     output reg wb_valid
61 );
62
63 `include "mips_define.vh"
64
65 // control signals
66 reg [1:0] exe_a_src_exe, exe_b_src_exe;
67 reg [3:0] exe_alu_oper_exe;
68 reg mem_ren_exe, mem_ren_mem;
69 reg mem_wen_exe, mem_wen_mem;
70 reg wb_data_src_exe, wb_data_src_mem, wb_data_src_wb;
71 reg fwd_m_exe, fwd_m_mem;
72
73 // IF signals
74 wire [31:0] inst_addr_next;
75
76 // ID signals
77 reg [31:0] inst_addr_id;
78 reg [31:0] inst_addr_next_id;
79 reg [4:0] regw_addr_id;
80 wire [4:0] addr_rs, addr_rt, addr_rd;
81 reg [31:0] data_rs_fwd, data_rt_fwd;
82 wire [31:0] data_rs, data_rt, data_imm;
83
84 // EXE signals
85 reg [31:0] inst_addr_exe;
86 reg [31:0] inst_addr_next_exe;
87 reg [31:0] inst_data_exe;
88 reg [31:0] data_rs_exe, data_rt_exe, data_imm_exe;
89 reg [31:0] opa_exe, opb_exe;
90 wire [31:0] alu_out_exe;
91
92 // MEM signals
93 reg [31:0] inst_addr_mem;
94 reg [31:0] inst_data_mem;
95 reg [31:0] data_rt_mem;
96 reg [31:0] alu_out_mem;
97
98 // WB signals
99 reg wb_wen_wb;
100 reg [31:0] alu_out_wb;
101 reg [31:0] mem_din_wb;
102 reg [4:0] regw_addr_wb;

```



```

103     reg [31:0] regw_data_wb;
104
105     // debug
106     `ifdef DEBUG
107     wire [31:0] debug_data_reg;
108     reg [31:0] debug_data_signal;
109
110     always @(posedge clk) begin
111         case (debug_addr[4:0])
112             0: debug_data_signal <= inst_addr;
113             1: debug_data_signal <= inst_data;
114             2: debug_data_signal <= inst_addr_id;
115             3: debug_data_signal <= inst_data_id;
116             4: debug_data_signal <= inst_addr_exe;
117             5: debug_data_signal <= inst_data_exe;
118             6: debug_data_signal <= inst_addr_mem;
119             7: debug_data_signal <= inst_data_mem;
120             8: debug_data_signal <= {27'b0, addr_rs};
121             9: debug_data_signal <= data_rs;
122             10: debug_data_signal <= {27'b0, addr_rt};
123             11: debug_data_signal <= data_rt;
124             12: debug_data_signal <= data_imm;
125             13: debug_data_signal <= opa_exe;
126             14: debug_data_signal <= opb_exe;
127             15: debug_data_signal <= alu_out_exe;
128             16: debug_data_signal <= 0;
129             17: debug_data_signal <= {16'b0, 2'b0, fwd_a_ctrl, 2'b0,
fwd_b_ctrl, 7'b0, fwd_m_ctrl};
130             18: debug_data_signal <= {19'b0, inst_ren, 7'b0, mem_ren, 3'b0,
mem_wen};
131             19: debug_data_signal <= mem_addr;
132             20: debug_data_signal <= mem_din;
133             21: debug_data_signal <= mem_dout;
134             22: debug_data_signal <= {27'b0, regw_addr_wb};
135             23: debug_data_signal <= regw_data_wb;
136             default: debug_data_signal <= 32'hFFFF_FFFF;
137         endcase
138     end
139
140     assign
141         debug_data = debug_addr[5] ? debug_data_signal : debug_data_reg;
142     `endif
143
144     // IF stage
145     assign
146         inst_addr_next = inst_addr + 4;
147
148     always @(*) begin
149         if_valid = ~if_rst & if_en;
150         inst_ren = ~if_rst;
151     end
152
153     always @(posedge clk) begin
154         if (if_rst) begin
155             inst_addr <= 0;
156         end
157         else if (if_en) begin
158             case (pc_src_ctrl)

```

```

159         PC_NEXT: inst_addr <= inst_addr_next;
160         PC_JUMP: inst_addr <= {inst_addr_id[31:28],
inst_data_id[25:0], 2'b0};
161         PC_JR: inst_addr <= data_rs_fwd;
162         PC_BRANCH: inst_addr <= inst_addr_next_id +
{data_imm[29:0], 2'b0};
163     endcase
164 end
165 end
166
167 // ID stage
168 always @(posedge clk) begin
169     if (id_rst) begin
170         id_valid <= 0;
171         inst_addr_id <= 0;
172         inst_data_id <= 0;
173         inst_addr_next_id <= 0;
174     end
175     else if (id_en) begin
176         id_valid <= if_valid;
177         inst_addr_id <= inst_addr;
178         inst_data_id <= inst_data;
179         inst_addr_next_id <= inst_addr_next;
180     end
181 end
182
183 assign
184     addr_rs = inst_data_id[25:21],
185     addr_rt = inst_data_id[20:16],
186     addr_rd = inst_data_id[15:11],
187     data_imm = imm_ext_ctrl ? {{16{inst_data_id[15]}}},
inst_data_id[15:0]} : {16'b0, inst_data_id[15:0]};
188
189 always @(*) begin
190     regw_addr_id = inst_data_id[15:11];
191     case (wb_addr_src_ctrl)
192         WB_ADDR_RD: regw_addr_id = addr_rd;
193         WB_ADDR_RT: regw_addr_id = addr_rt;
194         WB_ADDR_LINK: regw_addr_id = GPR_RA;
195     endcase
196 end
197
198 regfile REGFILE (
199     .clk(clk),
200     `ifdef DEBUG
201     .debug_addr(debug_addr[4:0]),
202     .debug_data(debug_data_reg),
203     `endif
204     .addr_a(addr_rs),
205     .data_a(data_rs),
206     .addr_b(addr_rt),
207     .data_b(data_rt),
208     .en_w(wb_wen_wb),
209     .addr_w(regw_addr_wb),
210     .data_w(regw_data_wb)
211 );
212
213 always @(*) begin

```

```

214     data_rs_fwd = data_rs;
215     data_rt_fwd = data_rt;
216     case (fwd_a_ctrl)
217         0: data_rs_fwd = data_rs;
218         1: data_rs_fwd = alu_out_exe;
219         2: data_rs_fwd = alu_out_mem;
220         3: data_rs_fwd = mem_din;
221     endcase
222     case (fwd_b_ctrl)
223         0: data_rt_fwd = data_rt;
224         1: data_rt_fwd = alu_out_exe;
225         2: data_rt_fwd = alu_out_mem;
226         3: data_rt_fwd = mem_din;
227     endcase
228     rs_rt_equal = (data_rs_fwd == data_rt_fwd);
229 end
230
231 // EXE stage
232 always @(posedge clk) begin
233     if (exe_rst) begin
234         exe_valid <= 0;
235         inst_addr_exe <= 0;
236         inst_data_exe <= 0;
237         inst_addr_next_exe <= 0;
238         regw_addr_exe <= 0;
239         exe_a_src_exe <= 0;
240         exe_b_src_exe <= 0;
241         data_rs_exe <= 0;
242         data_rt_exe <= 0;
243         data_imm_exe <= 0;
244         exe_alu_oper_exe <= 0;
245         mem_ren_exe <= 0;
246         mem_wen_exe <= 0;
247         wb_data_src_exe <= 0;
248         wb_wen_exe <= 0;
249         fwd_m_exe <= 0;
250         is_load_exe <= 0;
251     end
252     else if (exe_en) begin
253         exe_valid <= id_valid;
254         inst_addr_exe <= inst_addr_id;
255         inst_data_exe <= inst_data_id;
256         inst_addr_next_exe <= inst_addr_next_id;
257         regw_addr_exe <= regw_addr_id;
258         exe_a_src_exe <= exe_a_src_ctrl;
259         exe_b_src_exe <= exe_b_src_ctrl;
260         data_rs_exe <= data_rs_fwd;
261         data_rt_exe <= data_rt_fwd;
262         data_imm_exe <= data_imm;
263         exe_alu_oper_exe <= exe_alu_oper_ctrl;
264         mem_ren_exe <= mem_ren_ctrl;
265         mem_wen_exe <= mem_wen_ctrl;
266         wb_data_src_exe <= wb_data_src_ctrl;
267         wb_wen_exe <= wb_wen_ctrl;
268         fwd_m_exe <= fwd_m_ctrl;
269         is_load_exe <= is_load_ctrl;
270     end
271 end

```

```

272
273     always @(*) begin
274         opa_exe = data_rs_exe;
275         opb_exe = data_rt_exe;
276         case (exe_a_src_exe)
277             EXE_A_RS: opa_exe = data_rs_exe;
278             EXE_A_LINK: opa_exe = inst_addr_next_exe;
279         endcase
280         case (exe_b_src_exe)
281             EXE_B_RT: opb_exe = data_rt_exe;
282             EXE_B_IMM: opb_exe = data_imm_exe;
283             EXE_B_LINK: opb_exe = 32'h4; // linked address is the next one
of the delay slot
284         endcase
285     end
286
287     alu ALU (
288         .a(opa_exe),
289         .b(opb_exe),
290         .oper(exe_alu_oper_exe),
291         .result(alu_out_exe)
292     );
293
294     // MEM stage
295     always @(posedge clk) begin
296         if (mem_rst) begin
297             mem_valid <= 0;
298             inst_addr_mem <= 0;
299             inst_data_mem <= 0;
300             regw_addr_mem <= 0;
301             data_rt_mem <= 0;
302             alu_out_mem <= 0;
303             mem_ren_mem <= 0;
304             mem_wen_mem <= 0;
305             wb_data_src_mem <= 0;
306             wb_wen_mem <= 0;
307             fwd_m_mem <= 0;
308             is_load_mem <= 0;
309         end
310         else if (mem_en) begin
311             mem_valid <= exe_valid;
312             inst_addr_mem <= inst_addr_exe;
313             inst_data_mem <= inst_data_exe;
314             regw_addr_mem <= regw_addr_exe;
315             data_rt_mem <= data_rt_exe;
316             alu_out_mem <= alu_out_exe;
317             mem_ren_mem <= mem_ren_exe;
318             mem_wen_mem <= mem_wen_exe;
319             wb_data_src_mem <= wb_data_src_exe;
320             wb_wen_mem <= wb_wen_exe;
321             fwd_m_mem <= fwd_m_exe;
322             is_load_mem <= is_load_exe;
323         end
324     end
325
326     assign
327         mem_ren = mem_ren_mem,
328         mem_wen = mem_wen_mem,

```

```

329     mem_addr = alu_out_mem,
330     mem_dout = fwd_m_mem ? regw_data_wb : data_rt_mem;
331
332     // WB stage
333     always @(posedge clk) begin
334         if (wb_rst) begin
335             wb_valid <= 0;
336             wb_wen_wb <= 0;
337             wb_data_src_wb <= 0;
338             regw_addr_wb <= 0;
339             alu_out_wb <= 0;
340             mem_din_wb <= 0;
341         end
342         else if (wb_en) begin
343             wb_valid <= mem_valid;
344             wb_wen_wb <= wb_wen_mem;
345             wb_data_src_wb <= wb_data_src_mem;
346             regw_addr_wb <= regw_addr_mem;
347             alu_out_wb <= alu_out_mem;
348             mem_din_wb <= mem_din;
349         end
350     end
351
352     always @(*) begin
353         regw_data_wb = alu_out_wb;
354         case (wb_data_src_wb)
355             WB_DATA_ALU: regw_data_wb = alu_out_wb;
356             WB_DATA_MEM: regw_data_wb = mem_din_wb;
357         endcase
358     end
359
360 endmodule

```